

## UNIT: ELECTRICAL CIRCUITS

# ACT-BASED SCIENCE: SERIES VS. PARALLEL CIRCUITS – EFFICIENCY TEST (EXPERIMENTAL DESIGN & HYPOTHESIS TESTING)

These **hands-on science activities** align with **ACT Science College and Career Readiness Standards (CCRS)** and reinforce key skills like **data interpretation, experimental design, and scientific reasoning**—all while deepening students' understanding of **electric circuits**.

### ACT SKILLS PRACTICED:

- ✓ Designing & conducting experiments
- ✓ Evaluating multiple variables
- ✓ Interpreting scientific data

### OBJECTIVE:

Students will compare the efficiency and brightness of bulbs in **series vs. parallel circuits** and analyze which setup is better for practical applications.

### MATERIALS:

- Batteries (9V or AA)
- Light bulbs (small LED or incandescent)
- Wires & alligator clips
- Multimeters

### STUDENT DIRECTIONS:

#### Goal:

Compare the brightness, voltage, and current of light bulbs in series vs. parallel circuits. Use data to evaluate which setup is more efficient for real-world applications like home wiring.

## Part 1: Build and Test a Series Circuit

1. Set up your series circuit:
  - Connect the positive end of the battery to the first light bulb.
  - Connect the second light bulb in line with the first (end-to-end).
  - Connect the circuit back to the negative end of the battery.
  - Make sure the bulbs light up. If not, check connections.
2. Observe & record:
  - Look at the brightness of both bulbs. Are they dim or bright?
  - Write down your qualitative observation.
3. Measure with the multimeter:
  - Use the multimeter to measure:
    - Voltage across each bulb
    - Current in the entire circuit
  - Record your values in the data table.

## Part 2: Build and Test a Parallel Circuit

1. Set up your parallel circuit:
  - Connect the positive wire from the battery to both bulbs' positive terminals (using a Y-shaped wire split).
  - Do the same for the negative wire—connect both bulbs' negative terminals back to the battery.
  - Ensure both bulbs light up. If not, recheck wiring.
2. Observe & record:
  - Compare the brightness of both bulbs.
  - Are they brighter than before? The same? Record your observation.
3. Measure with the multimeter:
  - Measure:
    - Voltage across each bulb
    - Total current in the circuit
  - Write values in the table.

## Data Table

Circuit Type	Voltage (V) per Bulb	Current (A)	Brightness Observation
Series			
Parallel			

### Analysis & Discussion Questions:

Answer these questions in full sentences using your data.

1. How does bulb brightness compare between the series and parallel circuits?

→ \_\_\_\_\_  
→ \_\_\_\_\_

2. What did you notice about the voltage across each bulb in both circuits?

→ \_\_\_\_\_  
→ \_\_\_\_\_

3. How did the total current compare between the two circuits?

→ \_\_\_\_\_  
→ \_\_\_\_\_

4. Which circuit design is more efficient and why?

→ \_\_\_\_\_  
→ \_\_\_\_\_

5. Which design is more practical for home wiring? Explain.

→ \_\_\_\_\_  
→ \_\_\_\_\_

### ACT-STYLE DATA TABLE:

Circuit Type	Voltage (V) per Bulb	Current (A)	Brightness Observation
Series	?	?	?
Parallel	?	?	?

### DISCUSSION QUESTIONS:

- How does bulb brightness compare between series and parallel circuits?
- How does current differ between the two circuit types?
- Which circuit is more practical for home electrical wiring? Why?

## ACT-STYLE MULTIPLE CHOICE QUESTION:

- A student observes that light bulbs in a **series circuit** appear dimmer than those in a **parallel circuit**. What is the most likely explanation?
  - A. The series circuit provides more voltage to each bulb.
  - B. The parallel circuit provides each bulb with full voltage from the power source.
  - C. The current in the series circuit is higher than in the parallel circuit.
  - D. The series circuit allows for independent bulb operation.

## ☀ Why These ACT-Based Science Activities Matter

- ✓ Prepares students for **ACT Science** by reinforcing **data analysis, graph interpretation, and experimental design**.
- ✓ Develops **STEM inquiry skills**—helping students **think like scientists and engineers**.
- ✓ Connects **electrical circuits to real-world applications**, from home wiring to **renewable energy technologies**.