



UNIT: ELECTRICAL CIRCUITS

PIT CREW VOLTAGE CHECK – OHM’S LAW IN ACTION

OBJECTIVE:

Use Ohm’s Law to calculate current and resistance in a functioning circuit.

MATERIALS:

- ✓ Breadboard or circuit tray
- ✓ 9V battery + holder
- ✓ Assorted resistors (100Ω, 330Ω, 470Ω, 1kΩ)
- ✓ 2 LEDs
- ✓ Multimeter
- ✓ Jumper wires

STUDENT DIRECTIONS:

Step 1: Build Your Test Circuit

1. Connect the 9V battery to your breadboard.
2. Place two LEDs in series with one resistor.
3. Use jumper wires to connect the complete circuit.

Step 2: Measure Current and Voltage

1. Use the multimeter to measure voltage across the resistor.
2. Use the multimeter to measure current flowing through the circuit.
3. Record your results.

Step 3: Use Ohm’s Law

Use $V = IR$ to calculate the unknown value in your circuit:

- If you know V and R , solve for I .
- If you know V and I , solve for R .

Record Your Data:

Voltage (V)	Resistance (Ω)	Current (A)

Reflection Prompts:

- What happens to current if you increase the resistance?

- How does this relate to energy flow in a real race bike's system?

STANDARDS ALIGNMENT

NGSS: HS-PS3-1 **STEL:** STEL 1E, STEL 2E, STEL 3E, STEL 4E, STEL 5E, STEL 6E, STEL 7E **CCSS:**
CCSS.MATH.CONTENT.HSN.Q.A.1, CCSS.MATH.CONTENT.HSN.Q.A.2–3, CCSS.MATH.CONTENT.HSA.CED.A.1,
CCSS.MATH.CONTENT.HSA.REI.B.3, CCSS.MATH.PRACTICE.MP4, CCSS.MATH.PRACTICE.MP5