



UNIT: ELECTRICAL CIRCUITS

CIRCUIT LAYOUT GARAGE – SERIES VS. PARALLEL DESIGN

OBJECTIVE:

Build and compare series vs. parallel circuits.

MATERIALS:

- ✓ Breadboard or cardboard
- ✓ 2-3 LEDs
- ✓ Battery + holder
- ✓ Jumper wires
- ✓ Switch
- ✓ Resistors

STUDENT DIRECTIONS:

Step 1: Build a Series Circuit

1. Connect LEDs in a single path with resistors.
2. Test brightness and functionality.

Step 2: Build a Parallel Circuit

1. Wire each LED on its own branch to the power source.
2. Observe and record differences.

Compare:

Configuration	LED Brightness	What Happens If 1 LED Fails?
Series		
Parallel		

Reflection Prompts:

- Which layout is more energy-efficient? Why?

- How do real homes use parallel circuits for safety and efficiency?

STANDARDS ALIGNMENT

NGSS: HS-PS3-5 **STEL:** STEL 1E, STEL 2E, STEL 3E, STEL 4E, STEL 5E, STEL 6E, STEL 7E **CCSS:**
CCSS.MATH.CONTENT.HSN.Q.A.1–3, CCSS.MATH.CONTENT.HSA.CED.A.1, CCSS.MATH.CONTENT.HSA.REI.B.3,
CCSS.MATH.PRACTICE.MP2, CCSS.MATH.PRACTICE.MP4, CCSS.MATH.PRACTICE.MP5