

Name:	
Period:	

## UNIT: ELECTRICAL CIRCUITS

# CIRCUIT PUZZLE CHALLENGE

#### **OBJECTIVE:**

Create a circuit puzzle that only works when all paths are connected correctly.

#### **MATERIALS:**

- ✓ LEDs
- ✓ Buzzer
- ✓ Battery + holder
- ✓ Aluminum foil strips (or tape)
- ✓ Cardboard base
- ✓ Puzzle-shaped paper or cardboard pieces
- ✓ Wires or alligator clips
- √ Tape, scissors

#### STUDENT DIRECTIONS:

#### **Step 1: Create the Circuit Base**

- Lay foil strips on cardboard to form your "hidden path."
- Think like a game designer—leave gaps in the foil path where puzzle pieces will go!

#### **Step 2: Make Puzzle Connectors**

- Cut paper or cardboard into puzzle pieces that will bridge the gaps in your foil path.
- Tape foil to the bottom of each piece so it conducts electricity when placed correctly.

#### Step 3: Add LEDs and Buzzer

- Connect your circuit using the foil paths, puzzle bridges, battery, LED(s), and buzzer.
- Arrange the pieces so that the circuit is only complete—and works—when ALL puzzle pieces are in the right spot.

#### Step 4: Test It!

- Try placing puzzle pieces one at a time.
- Does the LED light up? Does the buzzer buzz?
- · What happens if a piece is missing or upside down?



Name:	
Period:	

#### **Test & Record:**

<b>Challenge Attempt</b>	Did It Work?	What Went Wrong (If Anything)?	
First Try	☐ Yes ☐ No		
Wrong Piece Used	☐ Yes ☐ No		
All Correct Pieces	☐ Yes ☐ No		
Can you design	a second puzzle	for another team to solve?	
  eflection:			
enection.			
<ul> <li>How does your</li> </ul>	puzzle model re	al-world circuit design challenges (like i	n electronics or
machines)?			

### STANDARDS ALIGNMENT

NGSS: MS-PS3-5 STEL: STEL 1B, STEL 2B, STEL 3B, STEL 4B, STEL 5B, STEL 6B, STEL 7B CCSS: CCSS.MATH.CONTENT.6.SP.B.4–5, CCSS.MATH.CONTENT.7.EE.B.3, CCSS.MATH.PRACTICE.MP1, CCSS.MATH.PRACTICE.MP7, CCSS.MATH.PRACTICE.MP7