



## UNIT: MEASUREMENT

# “POWER THE ARM” – VOLTAGE & ENERGY TRANSFER

### OBJECTIVE:

Use a multimeter to measure voltage in a circuit designed to “power” a part of the rover.

### GOAL:

You will build a simple LED circuit, use a multimeter to measure energy flow (voltage), and engineer a modification that lets the LED turn on only when a condition is met—just like powering a robotic arm on a rover!

### MATERIALS:

- ✓ Coin battery (CR2032 or similar)
- ✓ LED light
- ✓ Alligator clips or wire leads
- ✓ Paperclip (for a manual switch)
- ✓ Multimeter (with voltage and continuity modes)
- ✓ Optional: Resistor, tilt switch, or pressure sensor

### STUDENT DIRECTIONS:

#### Step 1: Build a Basic Circuit

1. Connect the **positive (+)** side of the coin battery to the **long leg (anode)** of the LED using wire or clips.
2. Connect the **short leg (cathode)** of the LED to the **negative (-)** side of the battery to complete the circuit.
3. Insert a **paperclip** between the circuit as a simple switch—pressing it completes the connection.

**Tip:** If the LED doesn't light, check your connections or reverse the LED legs.

**Step 2: Use the Multimeter****1. Measure Voltage Across the LED**

- Set your multimeter to DC voltage (V=).
- Place the red probe on the positive LED leg and black on the negative.
- Record the voltage:
  - Voltage across LED: \_\_\_\_\_ V

**2. Test Continuity of the Wires**

- Switch your multimeter to continuity mode ( 🔔 symbol).
- Touch both probes to each end of a wire.
- If it beeps, the wire conducts electricity well.

**3. (Optional) Measure Resistance of Components**

- Set your multimeter to  $\Omega$  (ohms).
- Test any resistors or other parts (like a pressure switch).
- Record the resistance value.

**Step 3: Engineering Challenge – Conditional Power**

**Your goal:** Modify your circuit so the LED turns on only when the “arm” moves or when a specific condition is met.

Choose one idea:

- Use a **tilt sensor** or a hanging paperclip that shifts when tilted
- Use a **pressure switch** (e.g., foil layers that connect only when pressed)
- Use your **paperclip switch** to close when a part of the rover moves

**Sketch or describe your design**

- My design idea: \_\_\_\_\_

## Reflection Questions:

- How does energy transfer from the battery to the LED in your circuit?

---

---

- What happened when you changed the materials or added a switch?

---

---

- Why might a real robotic arm need conditional circuits like this?

---

---

## STANDARDS ALIGNMENT

**NGSS:** HS-PS3-3 **STEL:** STEL 1E, STEL 2E, STEL 7F, STEL 8F, STEL 11F **CCSS:** CCSS.MATH.CONTENT.HSN.Q.A.1, CCSS.MATH.CONTENT.HSN.Q.A.3, CCSS.MATH.CONTENT.HSA.CED.A.2, CCSS.MATH.PRACTICE.MP4, CCSS.MATH.PRACTICE.MP5